

Institute of Engineering & Management
Department of Computer Science & Engineering
Computer Architecture Laboratory for 2nd year 4th semester 2018
Code: CS 493

Date: 07/04/2018

WEEK-7

Assignment 1: Implementation of Full Adder & Parallel Adder

Objective: Implement full adder using 2 half adder

Software used:

<u>Property Name</u>	<u>Value</u>
Device family	Spartan 3
Device	XC3S50
Package	PQ208
Speed	-5
Top-level source type	HDL
Synthesis Tool	XST(VHDL/Verilog)
Simulator	ISE Simulator
Preferred Language	VHDL

Theory:

- i. Make VHDL with required port specification.
- ii. Calculate the value c for both data flow and behavioral model using if and else statement with required condition.
- iii. Make test bench waveform and check for the given inputs.

Structural Model:

Code: HALF ADDER

```

begin
s<=a xor b;
c<=a and b;
end Behavioral;

```

OR GATE

```

begin
c<=a or b;
end Behavioral;

```


FULL ADDER

```

entity fa is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        cin : in STD_LOGIC;
        cout : out STD_LOGIC;
        sum : out STD_LOGIC);
end fa;
architecture Behavioral of fa is
  COMPONENT ha
    PORT(
      a : IN std_logic;
      b : IN std_logic;
      c : OUT std_logic;
      s : OUT std_logic
    );
  END COMPONENT;
  COMPONENT or1
    PORT(
      a : IN std_logic;
      b : IN std_logic;
      c : OUT std_logic
    );
  END COMPONENT;
  signal x: Std_logic;
  signal y: Std_logic;
  signal z: Std_logic;

begin
  a1: ha port map(a,b,x,y);
  a2: ha port map(cin,y,z,sum);
  a3: or1 port map(x,z,cout);
end Behavioral;

```

 Output:

Objective: Implement 4 bit Parallel adder using full adder

Software used:

<u>Property Name</u>	<u>Value</u>
Device family	Spartan 3
Device	XC3S50
Package	PQ208
Speed	-5
Top-level source type	HDL
Synthesis Tool	XST(VHDL/Verilog)
Simulator	ISE Simulator
Preferred Language	VHDL

Theory:

- i. Make VHDL with required port specification.
- ii. Calculate the value c for both data flow and behavioral model using if and else statement with required condition.
- iii. Make test bench waveform and check for the given inputs.

Code:

FULL ADDER

```
begin
s<= a xor b xor cin;
cout<= (a and b) or (b and cin) or (a and cin);
end Behavioral;
```

PARALLEL ADDER


```
entity pa1 is
  Port ( a1 : in STD_LOGIC_VECTOR (3 downto 0);
        b1 : in STD_LOGIC_VECTOR (3 downto 0);
        cin1 : in STD_LOGIC;
        sum : out STD_LOGIC_VECTOR (3 downto 0);
        carry : out STD_LOGIC);
end pa1;
```

```
architecture Behavioral of pa1 is
  COMPONENT fa
    PORT(
      a : IN std_logic;
      b : IN std_logic;
      cin : IN std_logic;
      s : OUT std_logic;
      cout : OUT std_logic
    );
  END COMPONENT;
```

```
signal x: STD_LOGIC_VECTOR (2 downto 0);
begin
e1: fa port map(a1(0),b1(0),cin1,sum(0),x(0));
e2: fa port map(a1(1),b1(1),x(0),sum(1),x(1));
e3: fa port map(a1(2),b1(2),x(1),sum(2),x(2));
e4: fa port map(a1(3),b1(3),x(2),sum(3),carry);
end Behavioral;
```

Structural Model:

Output:

 

Assignment 2: Implementation of 2:1 MUX and 4:1 MUX

Objective: Implement 2:1 Mux using AND, OR, NOT gate

Software used:

<u>Property Name</u>	<u>Value</u>
Device family	Spartan 3
Device	XC3S50
Package	PQ208
Speed	-5
Top-level source type	HDL
Synthesis Tool	XST(VHDL/Verilog)
Simulator	ISE Simulator
Preferred Language	VHDL

Theory:

- i. Make VHDL with required port specification.
- ii. Calculate the value c for both data flow and behavioral model using if and else statement with required condition.
- iii. Make test bench waveform and check for the given inputs.

Structural Model:

Code:

AND GATE

```
begin  
c<= a and b;  
end Behavioral;
```

OR GATE

```
begin  
c<=a or b;  
end Behavioral;
```

```
NOT GATE
begin
b<=not a;
end Behavioral;
```


```
MUX 2:1
entity mux21 is
  Port ( i : in  STD_LOGIC_VECTOR (1 downto 0);
        s : in  STD_LOGIC;
        o : out STD_LOGIC);
end mux21;
```

architecture Behavioral of mux21 is

```
  COMPONENT and1
  PORT(
    a : IN std_logic;
    b : IN std_logic;
    c : OUT std_logic
  );
  END COMPONENT;
  COMPONENT not1
  PORT(
    a : IN std_logic;
    b : OUT std_logic
  );
  END COMPONENT;
  COMPONENT or1
  PORT(
    a : IN std_logic;
    b : IN std_logic;
    c : OUT std_logic
  );
  END COMPONENT;
  signal x,y,z: STD_LOGIC;
```

```
begin
a1: and1 port map(s,i(1),x);
a2: not1 port map(s,z);
a3: and1 port map(z,i(0),y);
a4: or1 port map(x,y,o);
end Behavioral;
```

Output:

 

Objective: Implement 4:1 MUX using 2:1 MUX

Software used:

<u>Property Name</u>	<u>Value</u>
Device family	Spartan 3
Device	XC3S50
Package	PQ208
Speed	-5
Top-level source type	HDL
Synthesis Tool	XST(VHDL/Verilog)
Simulator	ISE Simulator
Preferred Language	VHDL

Theory:

- i. Make VHDL with required port specification.
- ii. Calculate the value c for both data flow and behavioral model using if and else statement with required condition.
- iii. Make test bench waveform and check for the given inputs.

Structural Model:

Code:

MUX 2:1

```
begin
o<=((not s) and i0) or (s and i1);
end Behavioral;
```

MUX 4:1

```
entity mux41 is
  Port ( i : in  STD_LOGIC_VECTOR (3 downto 0);
        ss : in  STD_LOGIC_VECTOR (1 downto 0);
        outp : out STD_LOGIC);
end mux41;
```

architecture Behavioral of mux41 is

```
  COMPONENT mux21
  PORT(
    i0 : IN std_logic;
    i1 : IN std_logic;
    s  : IN std_logic;
    o  : OUT std_logic
  );
  END COMPONENT;
  signal x,y,z: STD_LOGIC;
begin
  a1: mux21 port map(i(0),i(1),ss(0),x);
  a2: mux21 port map(i(2),i(3),ss(0),y);
  a3: mux21 port map(x,y,ss(1),outp);
end Behavioral;
```

Output:

