

**Institute of Engineering & Management**  
**Department of Computer Science & Engineering**  
**Communication Engineering Laboratory for 2<sup>nd</sup> year 4<sup>th</sup> semester 2018**  
**Code: CS 491**

**Date: 22/02/18**

**ASSIGNMENT- 6**

**Experiment Name:** Design a monostable multivibrator using 555 timer

**Theory:** A monostable multivibrator (MMV) often called a one-shot multivibrator, is a pulse generator circuit in which the duration of the pulse is determined by the R-C network, connected externally to the 555 timer.

**Circuit Diagram:**

**Operation of the circuit:** Initially, when the output at pin 3 is low i.e. the circuit is in a stable state, the transistor is on and capacitor- C is shorted to ground. When a negative pulse is applied to pin 2, the trigger input falls below  $+1/3 V_{CC}$ , the output of comparator goes high which resets the flip-flop and consequently the transistor turns off and the output at pin 3 goes high. This is the transition of the output from stable to quasi-stable state, as shown in figure. As the discharge transistor is cutoff, the capacitor C begins charging toward  $+V_{CC}$  through resistance  $R_A$  with a time constant equal to  $R_A C$ . When the increasing capacitor voltage becomes slightly greater than  $+2/3 V_{CC}$ , the output of comparator 1 goes high, which sets the flip-flop. The transistor goes to saturation, thereby discharging the capacitor C and the output of the timer goes low, as illustrated in figure. **Thus the output returns back to stable state from quasi-stable state.** The output of the Monostable Multivibrator remains low until a trigger pulse is again applied. Then the cycle repeats. Trigger input and output voltage are shown in figure.

The time during which the timer output remains high is given as  $t_p = 1.0986 R_A C$  where  $R_A$  is in ohms and C is in farads.


**Name: Ranajit Roy, Sec: A, Roll: 47**

**Observation Table:**

$$DC = 88.3\%$$

$$T_{trg} = (1/f) * (1-DC) \\ = (1/10) * (1-(88.3/100))$$

No. of Obs.	R	Calculated value of T	Oscilloscope Value	
			T	V <sub>out</sub>

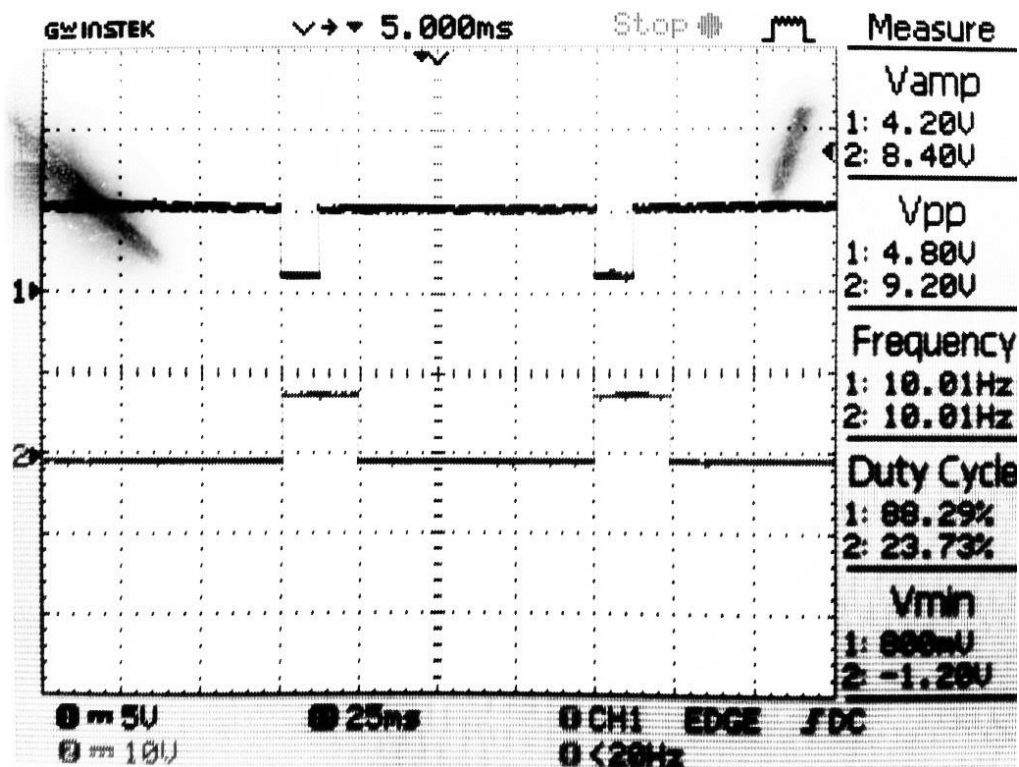**Waveform:**

**Conclusion:** In this experiment we have implemented monostable multivibrator using IC 555 timer circuit.